 


clk_div


RATIO = 4

```
# Loading work.clk_div_tb(tb)
# Loading work.clk_div(str)
# Loading work.counter(bhv)
VSIM 87> run -all
# Break key hit
# Break key hit
# Break in Architecture tb at C:/Users/Nick/Documents/Spring 2016/EEL 4712/Digital-Design-Labs/Lab-4/clk_gen/clk_div_tb.vhd line 41
VSIM 88>
```




RATIO = 2
 
```
# Loading work.clk_div_tb(tb)
# Loading work.clk_div(str)
# Loading work.counter(bhv)
VSIM 85> run -all
# Break key hit
# Break in Process line__30 at C:/Users/Nick/Documents/Spring 2016/EEL 4712/Digital-Design-Labs/Lab-4/clk_gen/counter.vhd line 30
VSIM 86>
```



clk_gen

```
# Loading work.clk_gen_tb(tb)
# Loading work.clk_gen(str)
# Loading work.clk_div(str)
# Loading work.counter(bhv)
VSIM 142> run -all
# ** Note: DONE!
# Time: 14000090 ns Iteration: 4 Instance: /clk_gen_tb
VSIM 143>
```

 

gray1

```
# vsim work.gray1_tb
# Loading std.standard
# Loading ieee.std_logic_1164(body)
# Loading work.gray1_tb(tb)
# Loading work.gray1(bhv)
VSIM 52> run -all
# ** Note: SIMULATION FINISHED!
#   Time: 10195 ns  Iteration: 0  Instance: /gray1_tb

VSIM 53>
```



gray2


```
# vsim work.gray2_tb
# Loading std.standard
# Loading ieee.std_logic_1164(body)
# Loading work.gray2_tb(tb)
# Loading work.gray2(bhv)
VSIM 55> run -all
# ** Note: SIMULATION FINISHED!
#   Time: 10195 ns  Iteration: 0  Instance: /gray2_tb

VSIM 56>
```



counter
 
```
# vsim work.counter_tb
# Loading std.standard
# Loading ieee.std_logic_1164(body)
# Loading ieee.numeric_std(body)
# Loading work.counter_tb(tb)
# Loading work.counter(bhv)
VSIM 58> run -all
# ** Note: SIMULATION FINISHED!
#   Time: 445 ns   Iteration: 0   Instance: /counter_tb
VSIM 59>
```



top_level

The `top_level` entity is nothing more than an in-depth structural architecture. It creates instances of `decoder7seg` for each LED, and instances of `clk_gen`, `gray2`, and `counter`. It also defines signals and constants as necessary for internal connections. The specific connections it provides are: input 50MHz `clk` goes to `clk_gen` and is converted to the 1Hz `clk`, and passed as `clk_gen_out`. This signal is given as inputs to the `clk` of `gray2` and `counter`. The output of `gray2` is connected to LED3, and the output of the counter is connected to LED2, while the remaining LEDs are set to a constant 0. The three non-decoder entities all receive the same `rst` signal, which is the overall input `rst`. The counter also receives `up_n` and `load_n` from the remaining buttons (1 and 0, respectively), and receives its input signal from `switches[9..6]`.